

Computer Architecture and Organization

September 2nd, 2015

Administrative Information

Administrative Information

- Take the department's course survey
<https://goo.gl/grdu9M>

Administrative Information

- Take the department's course survey
<https://goo.gl/grdu9M>
- There *is* a reading journal for Friday. You can find the reading in eReserve.


Administrative Information

- Take the department's course survey
<https://goo.gl/grdu9M>
- There *is* a reading journal for Friday. You can find the reading in eReserve.
- I will be gone Friday and Monday. Jerod Weinman will be teaching those days.


Administrative Information

- Take the department's course survey
<https://goo.gl/grdu9M>
- There *is* a reading journal for Friday. You can find the reading in eReserve.
- I will be gone Friday and Monday. Jerod Weinman will be teaching those days.
- Assignment 1 is due next Monday at 10:30pm.

Name That Gate!

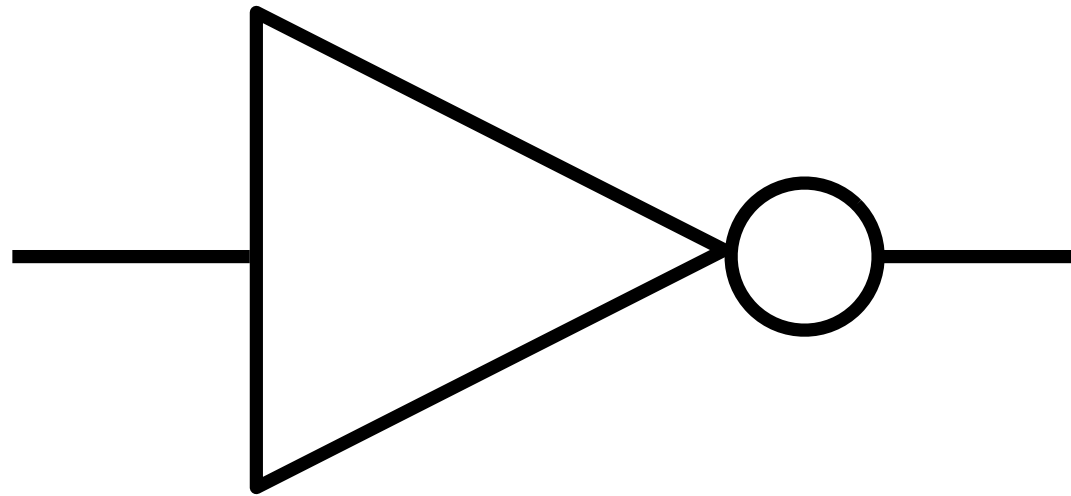


Name That Gate!

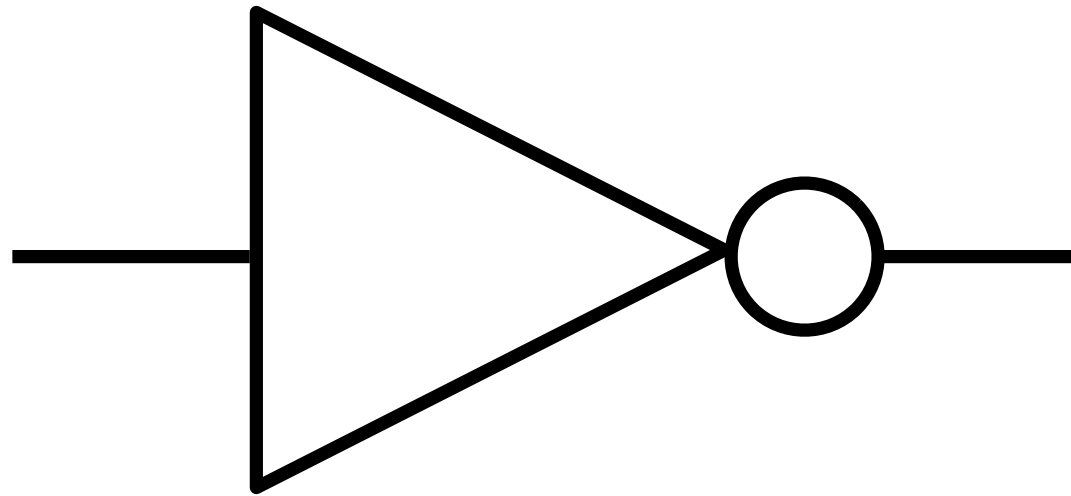


NOT

Name That Gate!

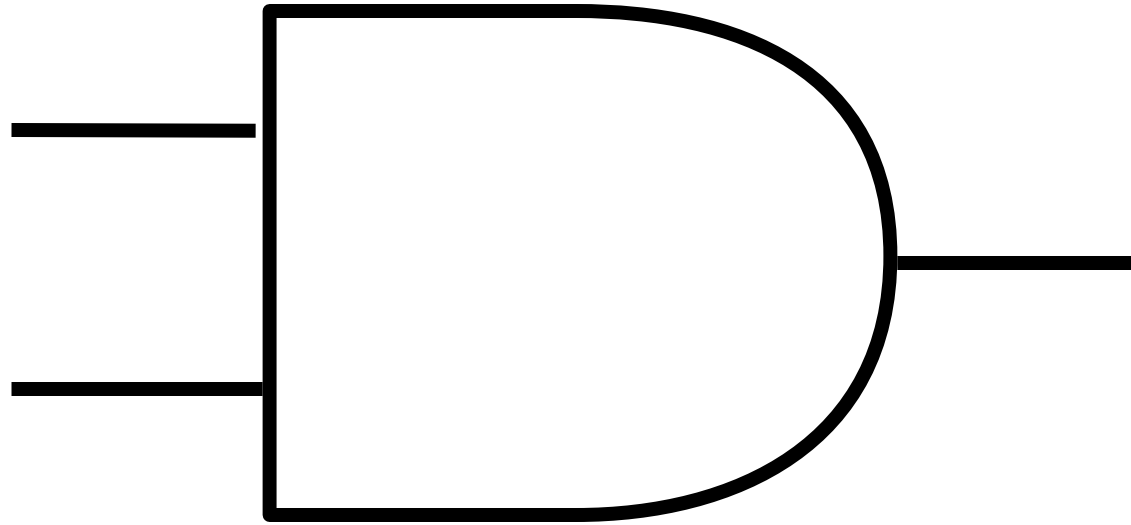


Name That Gate!

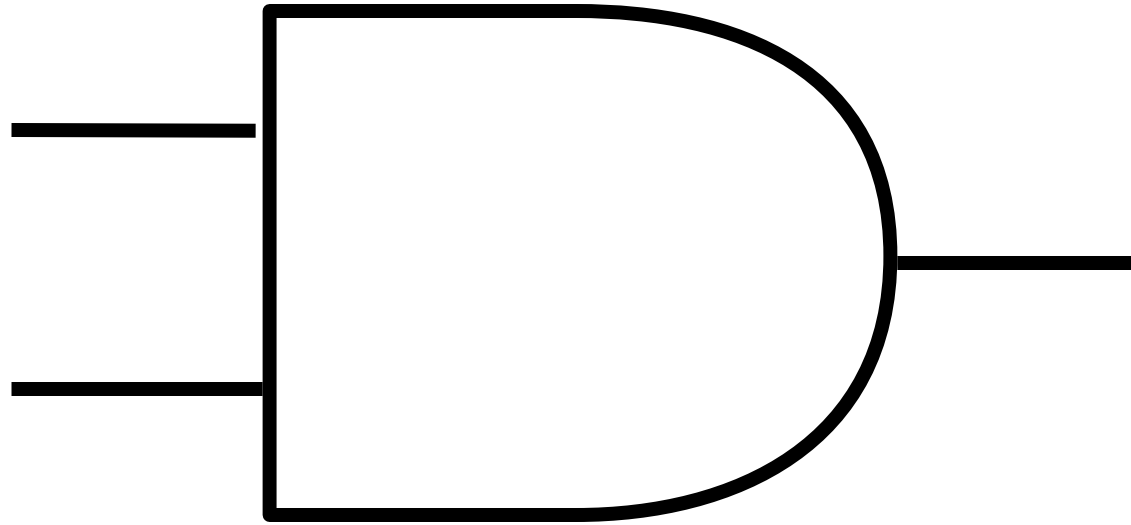


AND

Name That Gate!

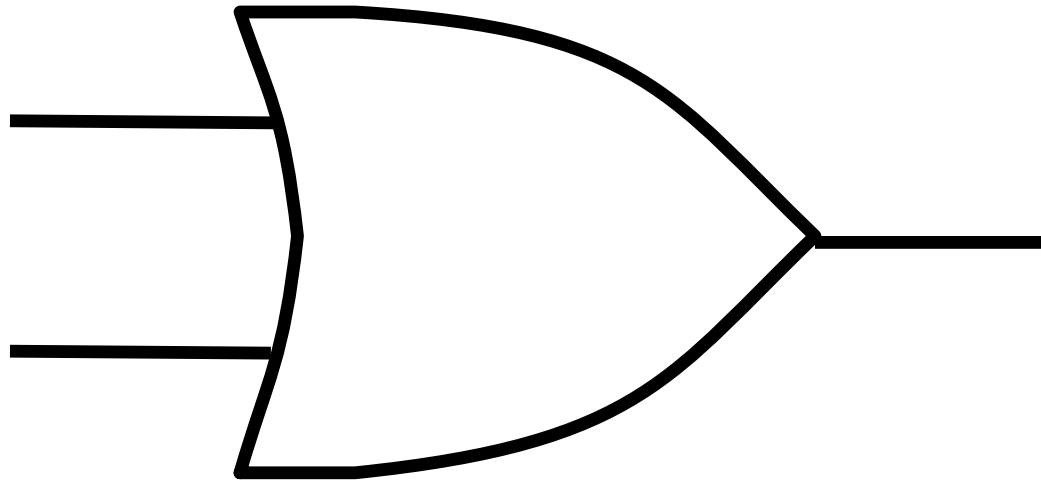


Name That Gate!

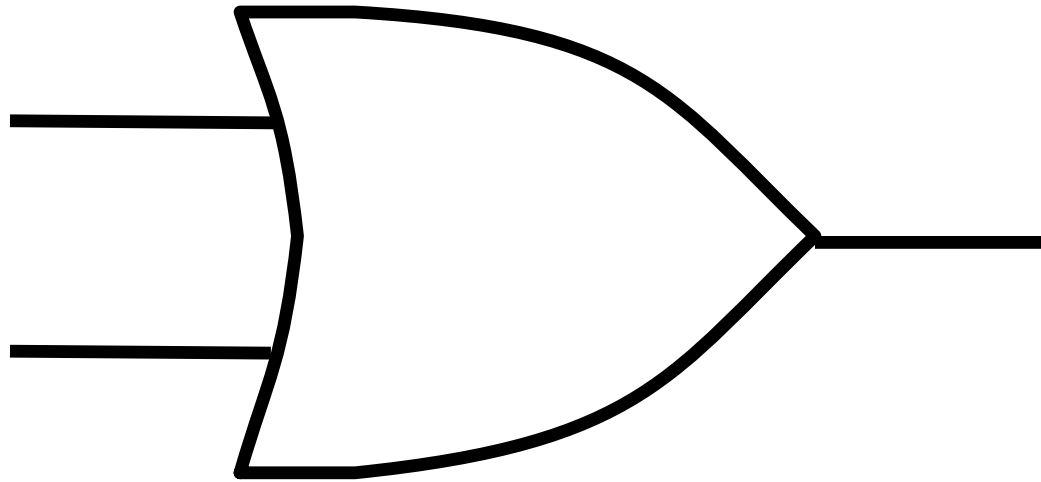


OR

Name That Gate!

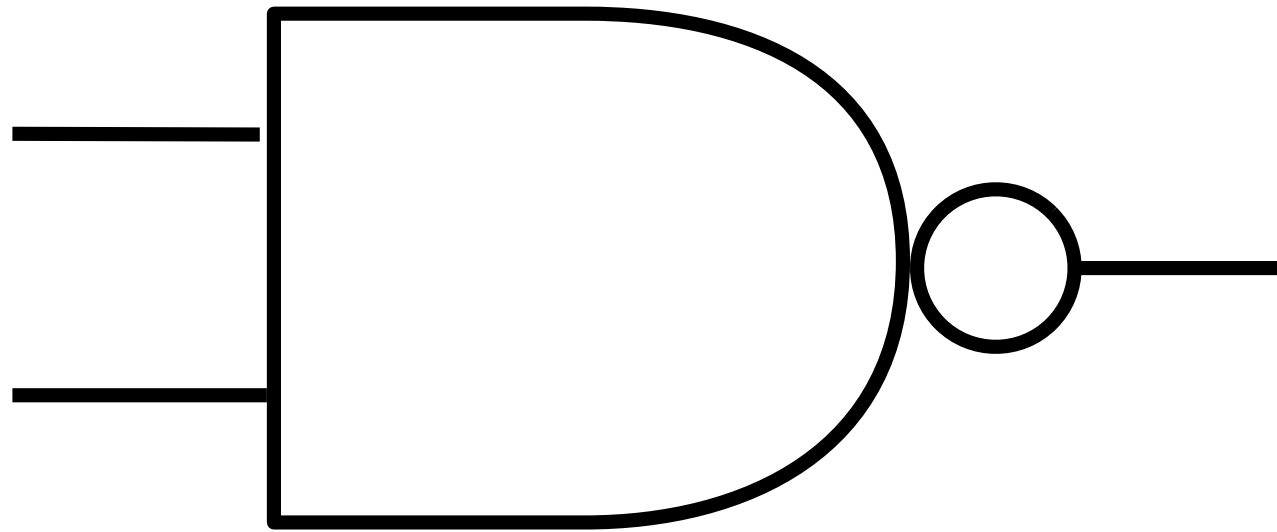


Name That Gate!

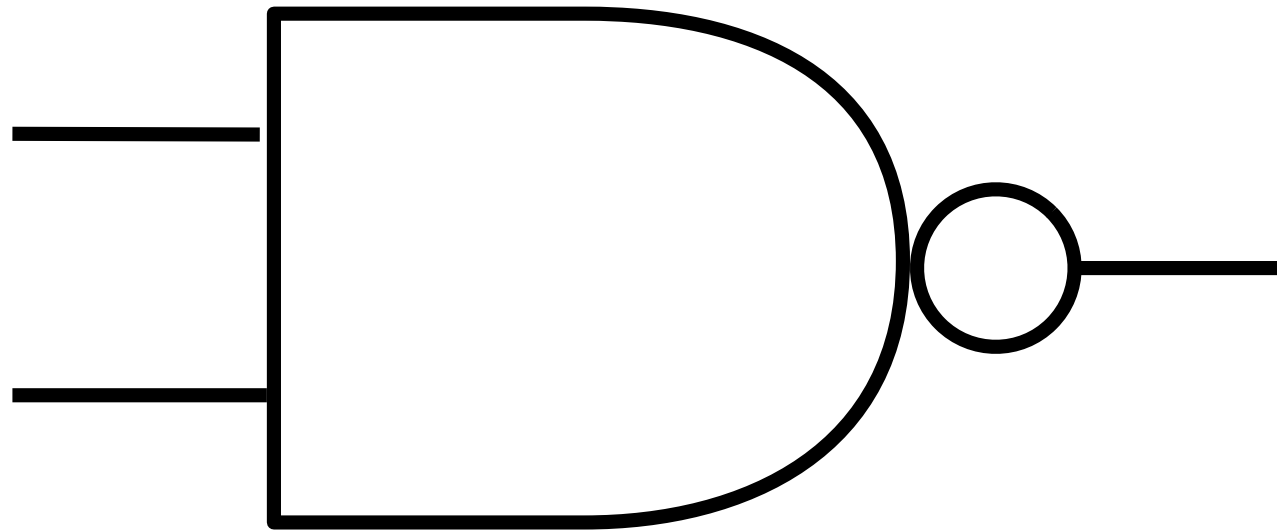


NAND

Name That Gate!

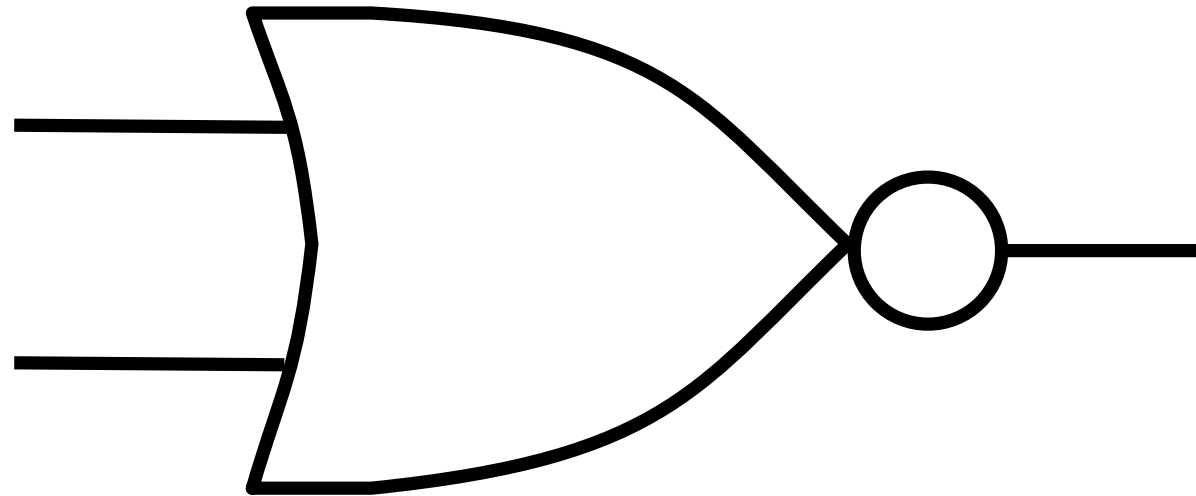


Name That Gate!

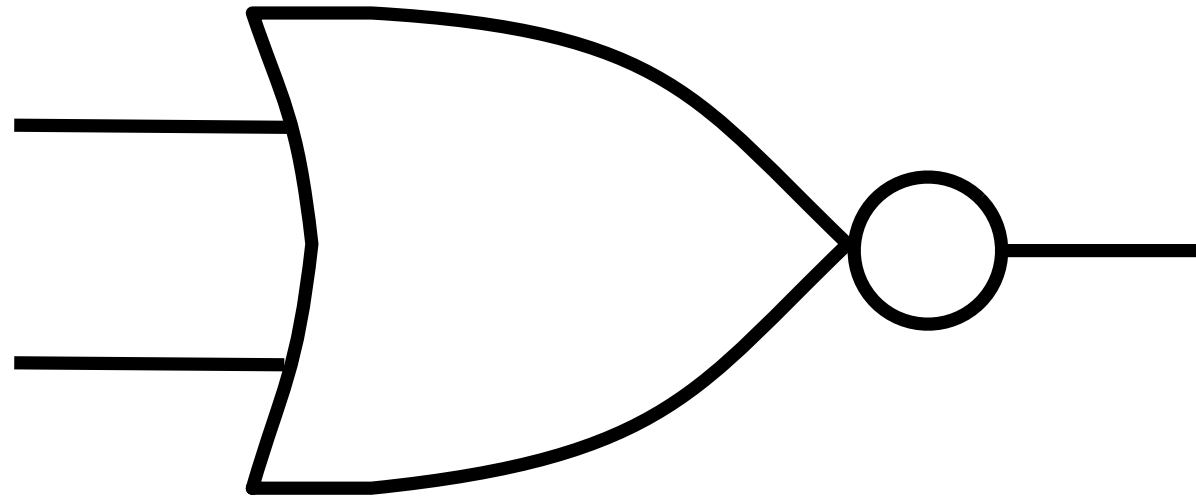


NOR

Name That Gate!

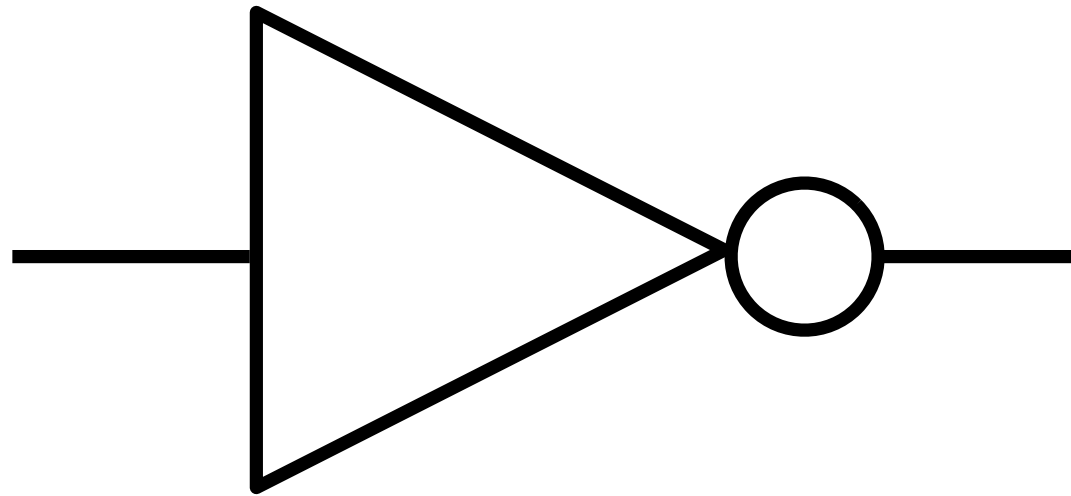


Name That Gate!

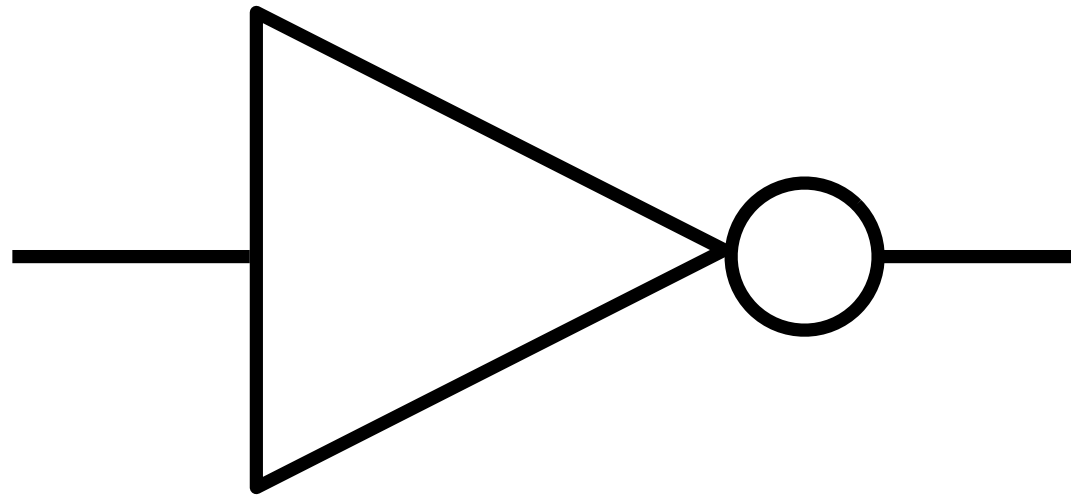


NOT

Name That Gate!

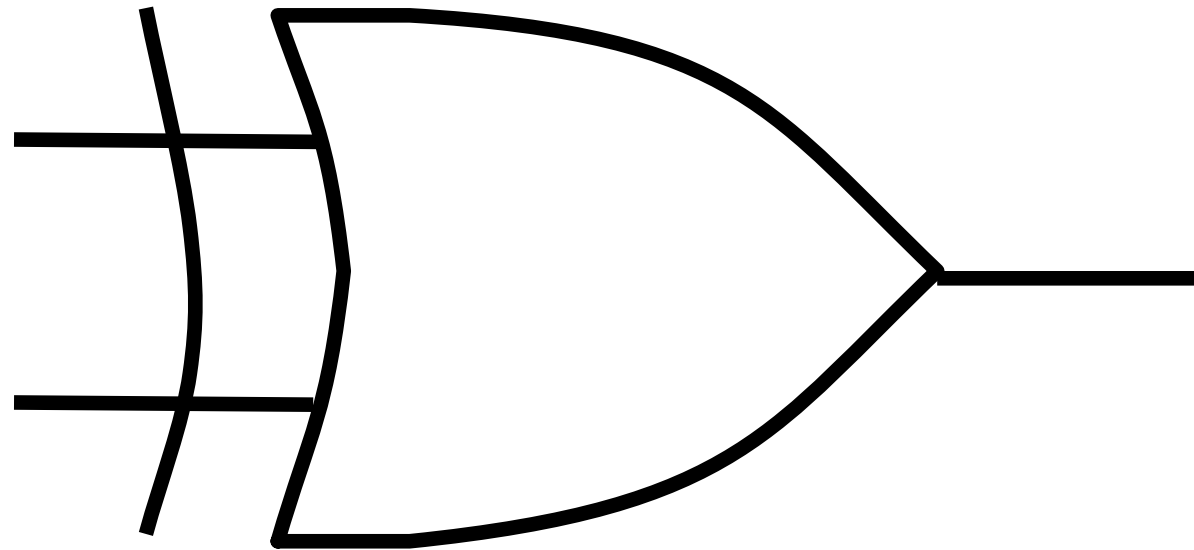


Name That Gate!

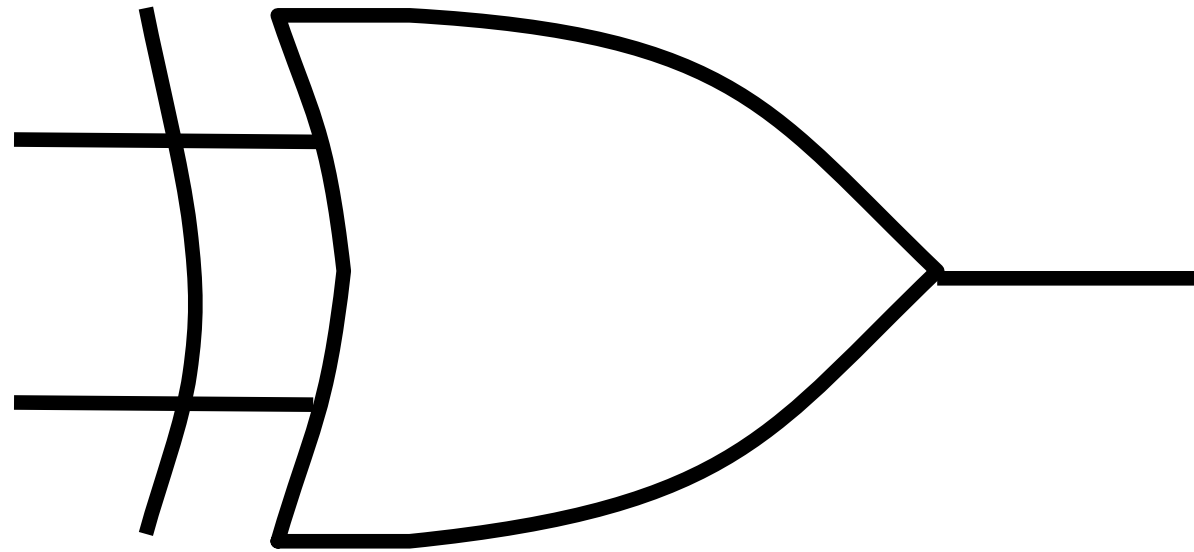


XOR

Name That Gate!

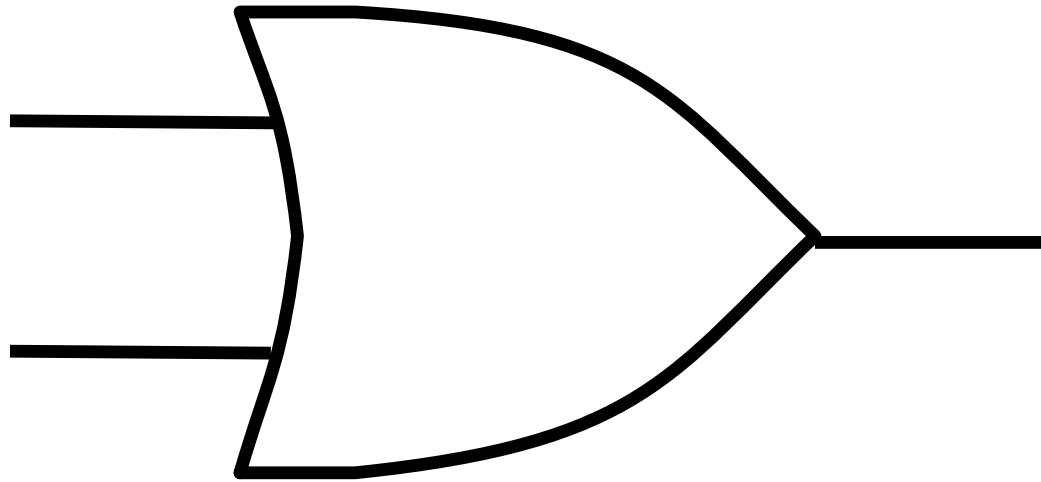


Name That Gate!

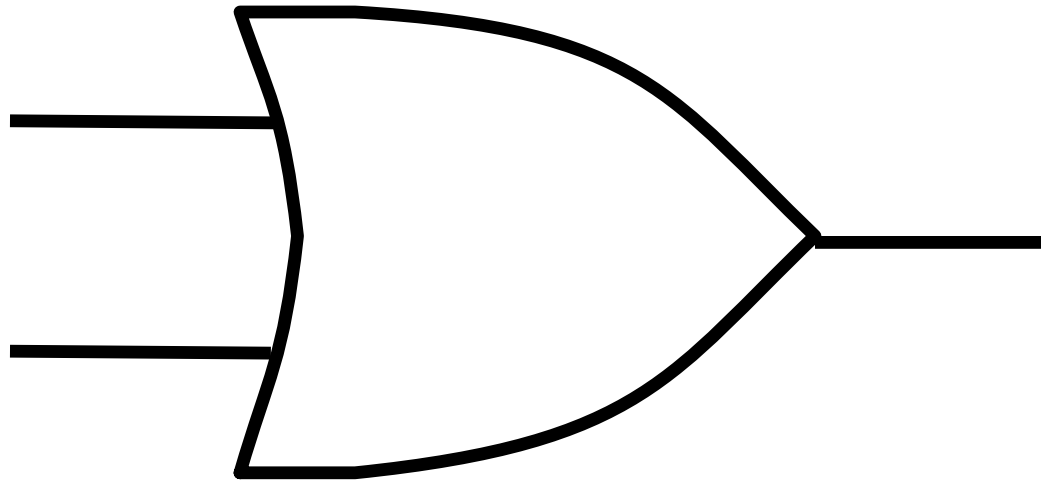


OR

Name That Gate!







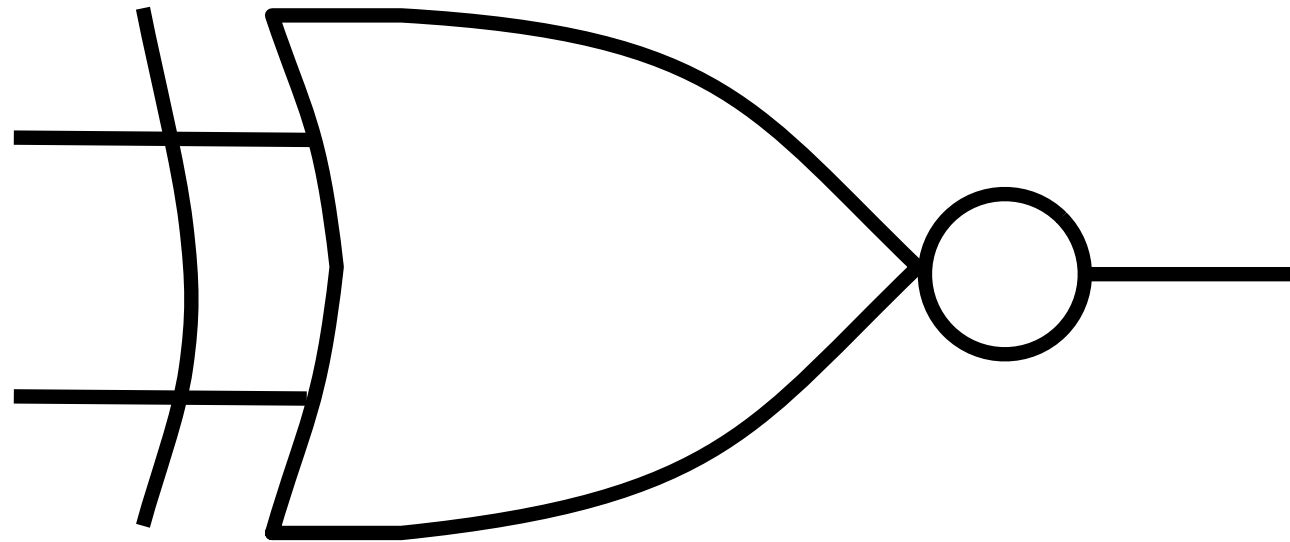


Name That Gate!

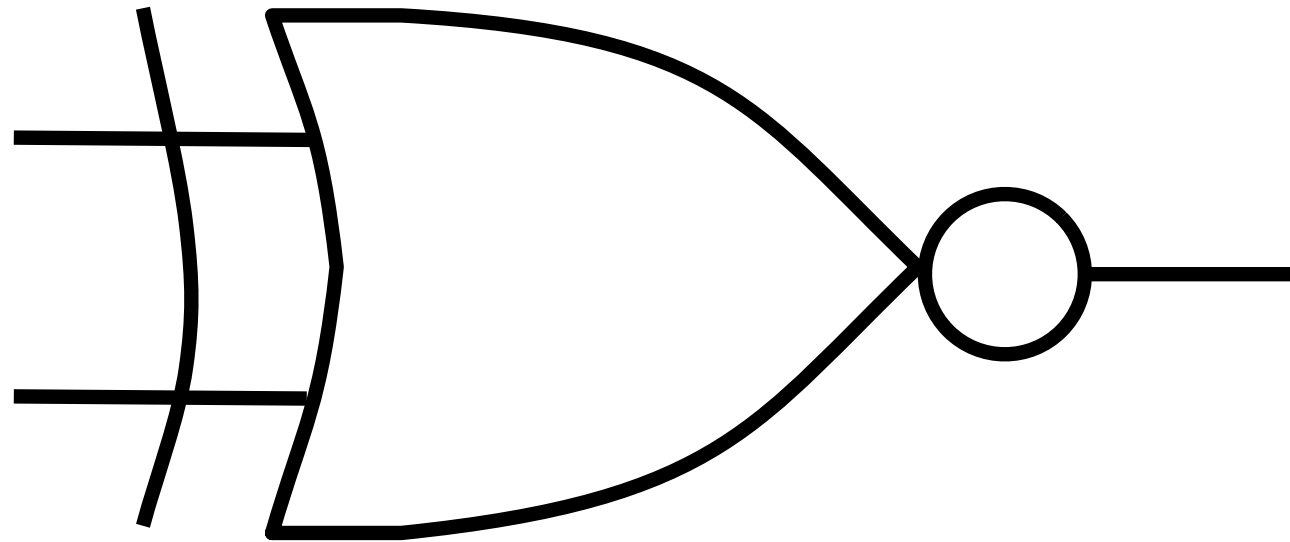


XNOR


How will we remember these?

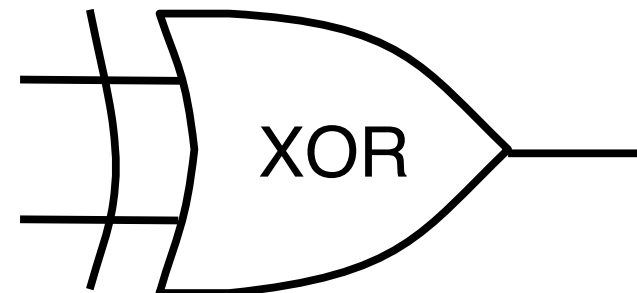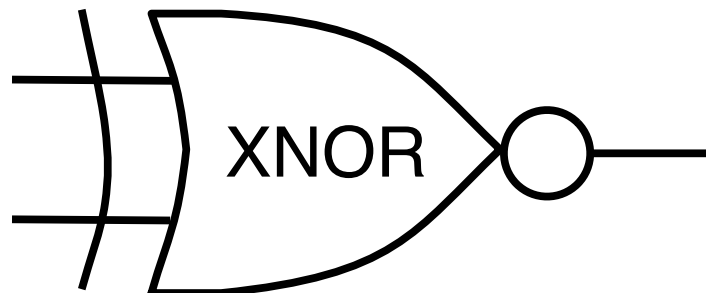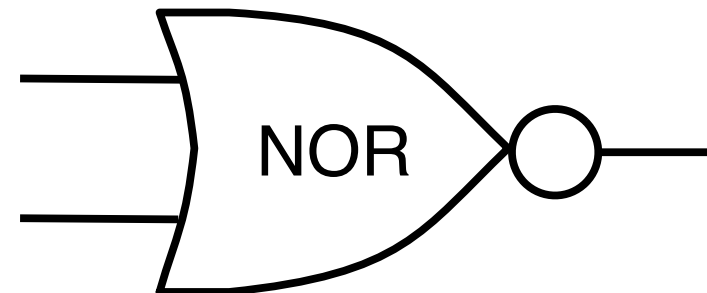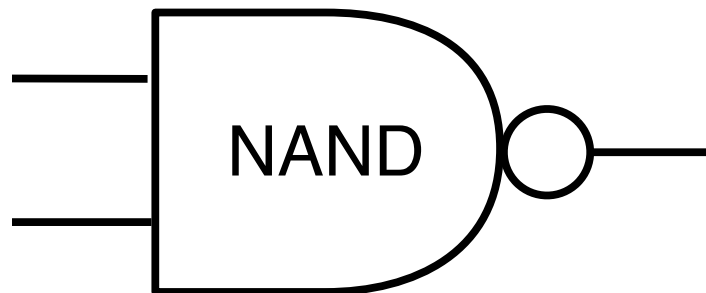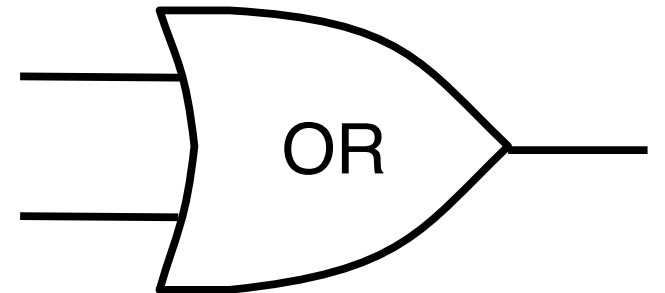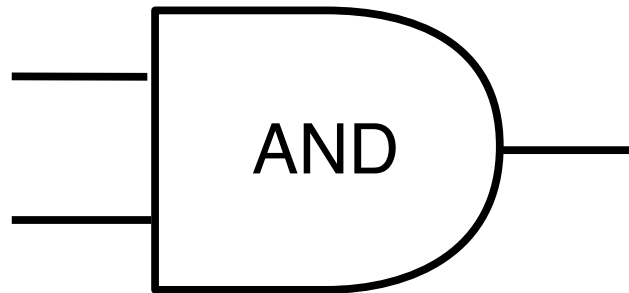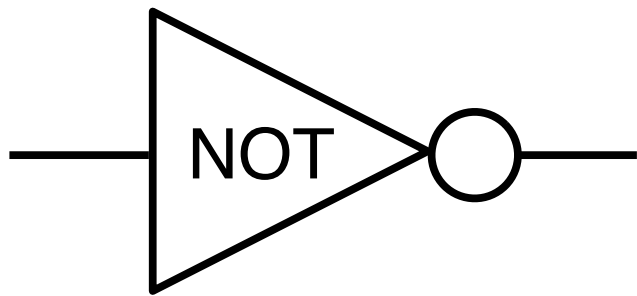


Build That Gate!

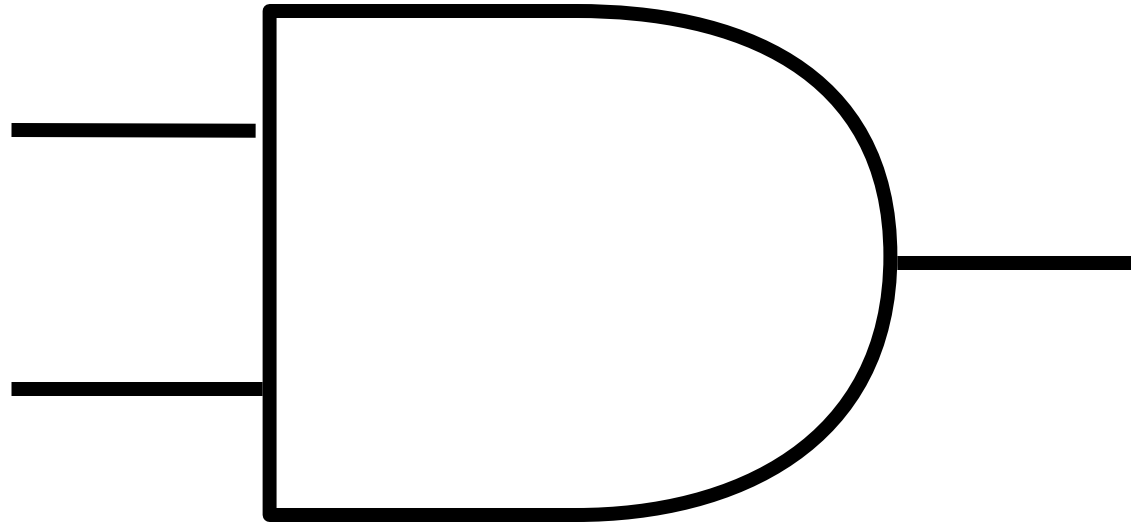

Build That Gate!

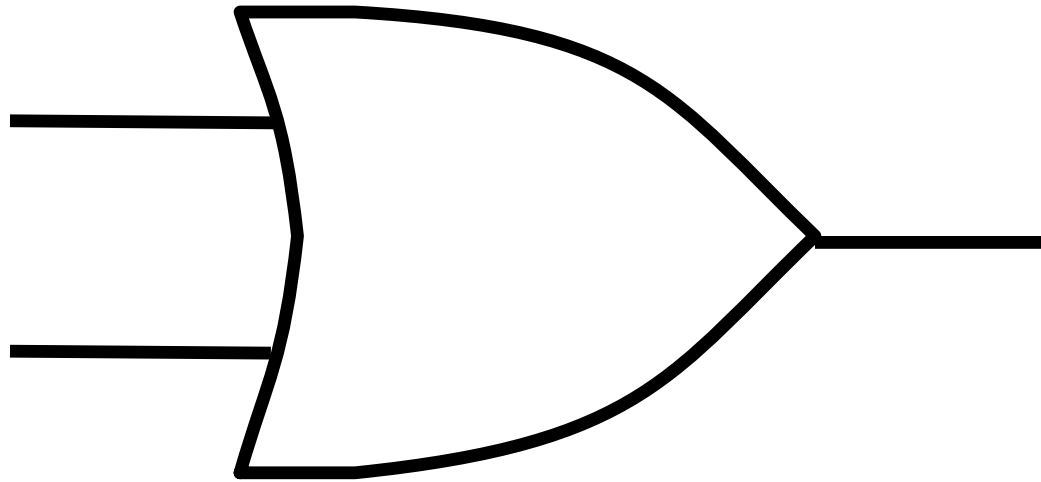

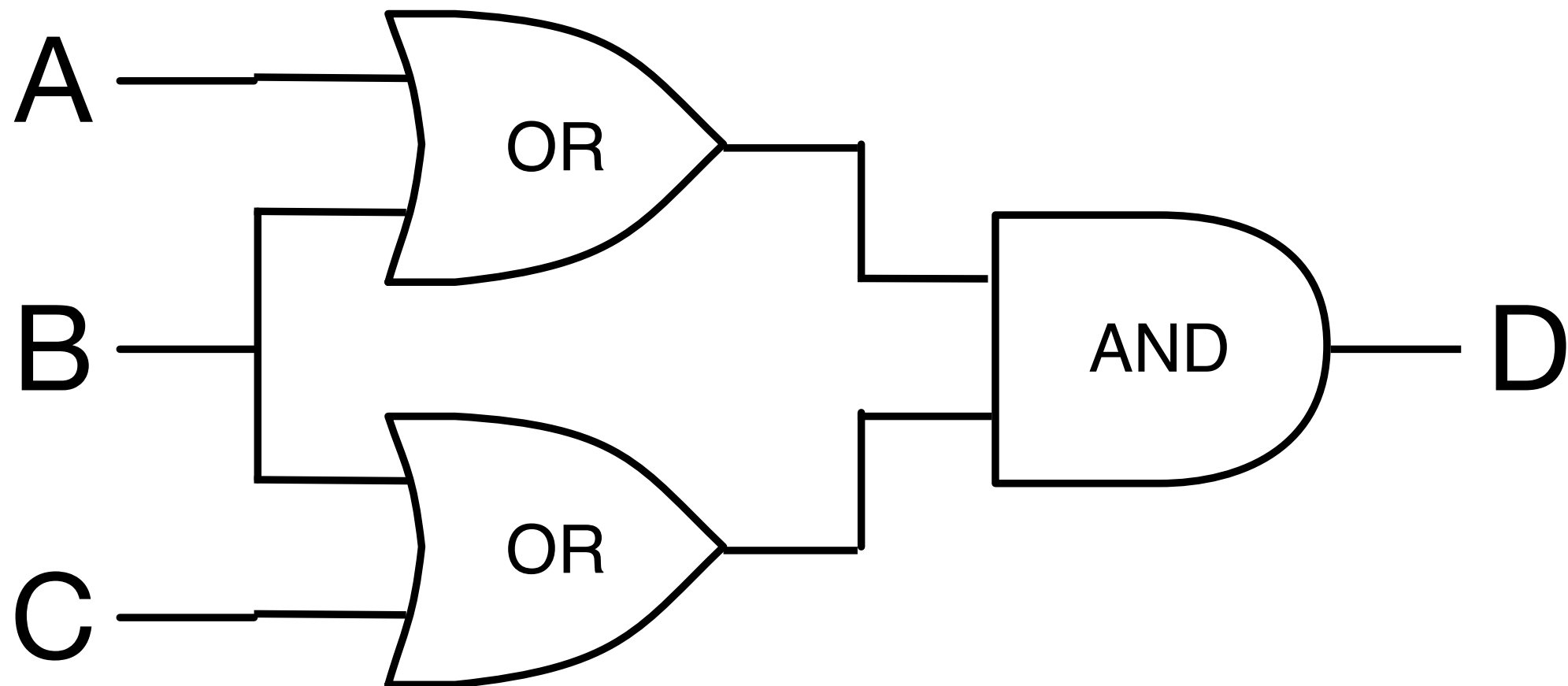
What is the truth table for this circuit?



Draw a circuit for this truth table

A	B	C
0	0	0
0	1	1
1	0	0
1	1	1

Draw a circuit for this truth table

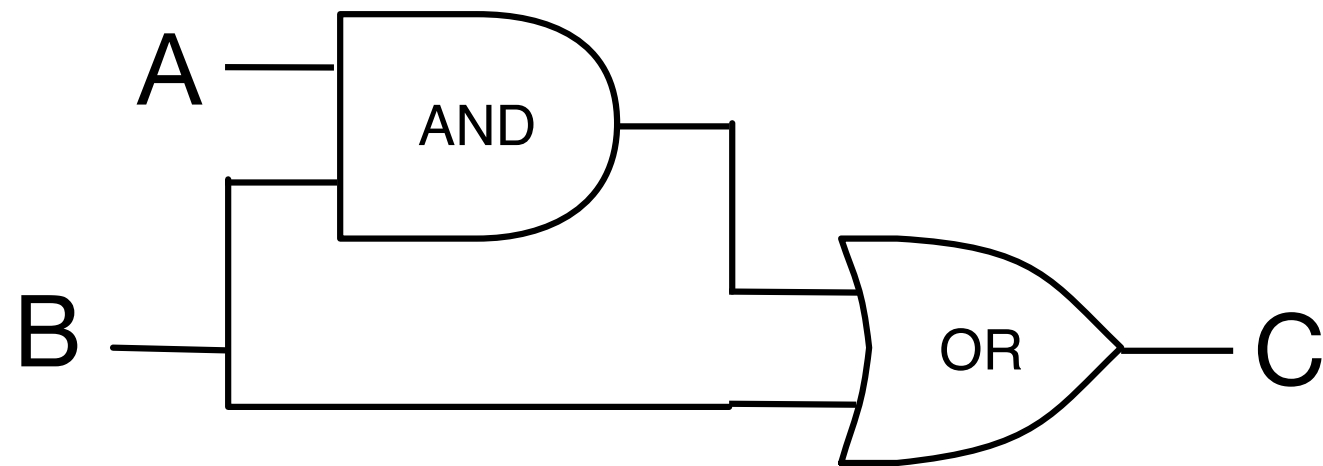


A	B	C
0	0	0
0	1	1
1	0	0
1	1	1

Draw a circuit for this truth table


A	B	C	D
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

Draw a circuit for this truth table

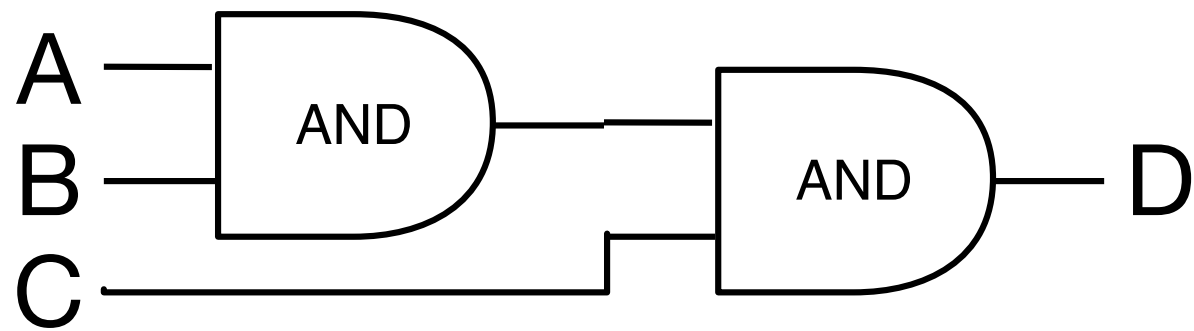


A	B	C	D
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1


A tricky one

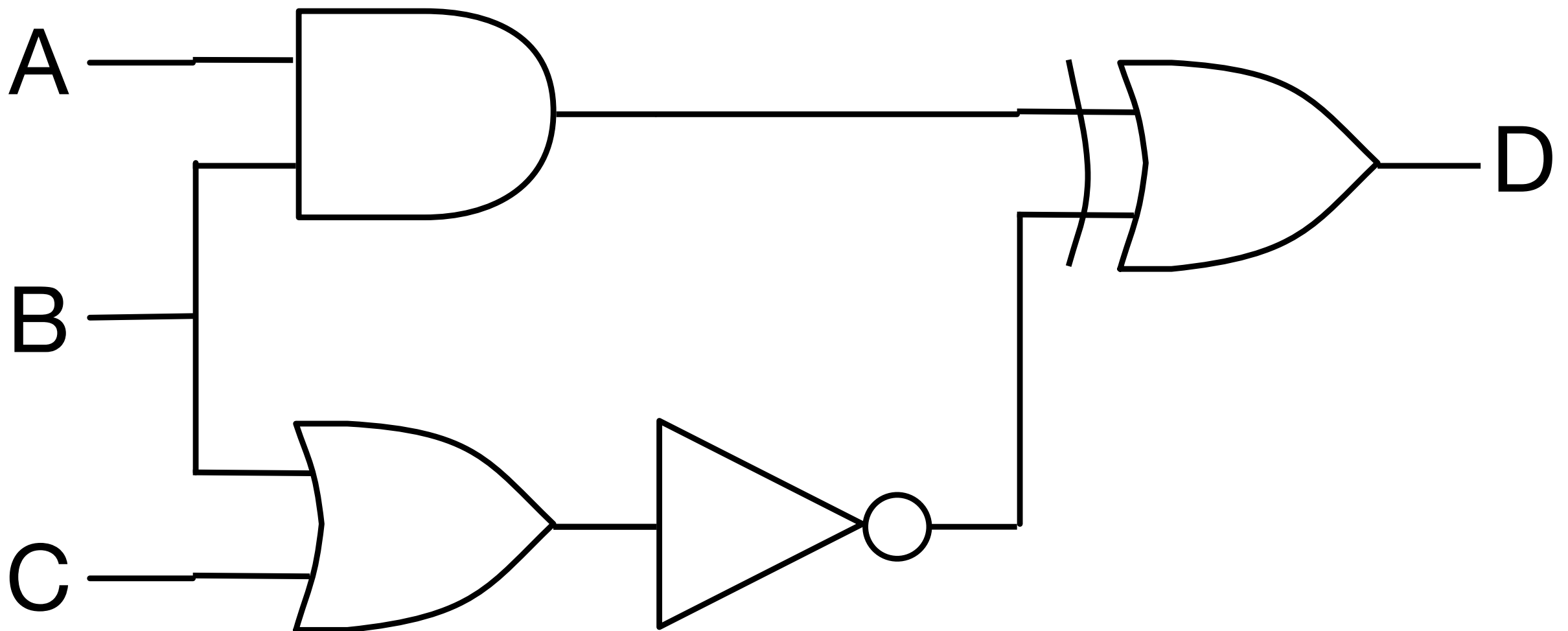

A tricky one

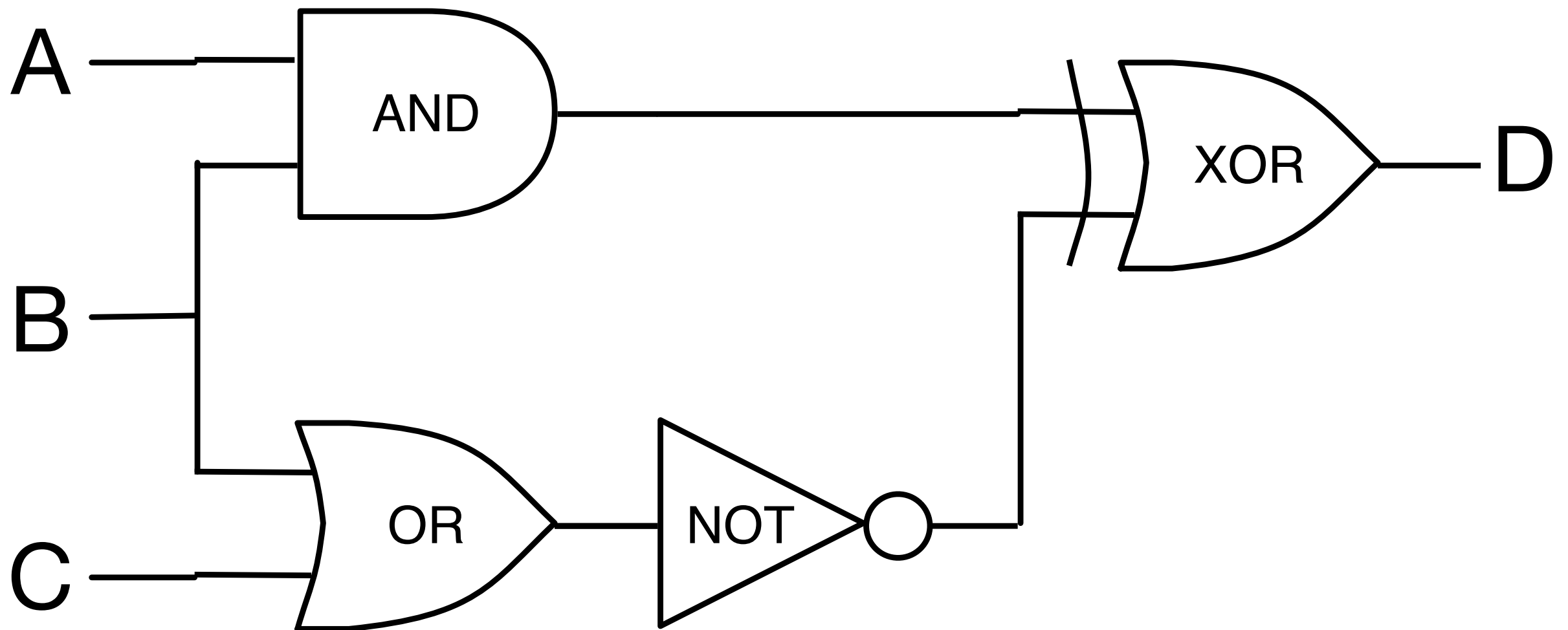

A tricky one

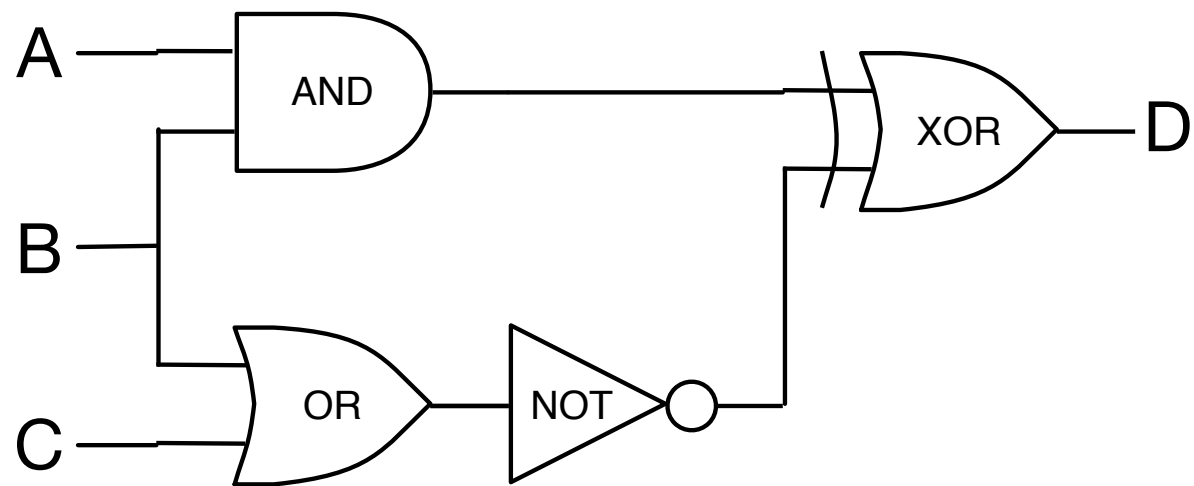

A	B	C	D
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

Bubble Pushing

On the board

Reminders

- Take the department's course survey
<https://goo.gl/grdu9M>
- There *is* a reading journal for Friday. You can find the reading in eReserve.
- I will be gone Friday and Monday. Jerod Weinman will be teaching those days.
- Assignment 1 is due next Monday at 10:30pm.